



# **Assignment.3**

## **Network Theory**

### **Sheet.2-Problem.9**

Student Name: Ahmed Ayman Ahmed Hassan

Student Code: 1700037

Section: 1



## • Analytical Solution:

4-Port Network S-parameters

$$\begin{bmatrix} V_1^- \\ V_2^- \\ V_3^- \\ V_4^- \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} & S_{13} & S_{14} \\ S_{21} & S_{22} & S_{23} & S_{24} \\ S_{31} & S_{32} & S_{33} & S_{34} \\ S_{41} & S_{42} & S_{43} & S_{44} \end{bmatrix} \begin{bmatrix} V_1^+ \\ V_2^+ \\ V_3^+ \\ V_4^+ \end{bmatrix}$$

① To Get  $T = \frac{V_4^-}{V_1^+}$  ?? we have  $\Rightarrow \Gamma = \frac{V_2^+}{V_2^-} = \frac{V_3^+}{V_3^-} \neq$

$V_4^- = S_{41} V_1^+ + S_{42} V_2^+ + S_{43} V_3^+ + S_{44} V_4^+ \quad (a) \quad (\text{Port 4 matched } \text{load } V_4^+ = 0)$

From  $[S]$  of Hybrid network  $\Rightarrow \begin{cases} V_2^- = S_{21} V_1^+ = \frac{-j}{\sqrt{2}} V_1^+ \\ V_3^- = S_{31} V_1^+ = \frac{-1}{\sqrt{2}} V_1^+ \end{cases}$

So we have the following ::

$\left( V_2^+ = \frac{-j}{\sqrt{2}} \Gamma V_1^+ \quad V_3^+ = \frac{-1}{\sqrt{2}} \Gamma V_1^+ \right) \Rightarrow \text{Sub. in (a)}$

$\therefore V_4^- = -\frac{1}{\sqrt{2}} \cdot \frac{-j}{\sqrt{2}} \Gamma V_1^+ + \frac{-j}{\sqrt{2}} \cdot \frac{-1}{\sqrt{2}} \Gamma V_1^+ = j \Gamma V_1^+$

$\therefore \boxed{T = \frac{V_4^-}{V_1^+} = j \Gamma} \neq$

② To show matching at port 1 ?? Prove  $(V_1^- = 0)$

$V_1^- = S_{11} V_1^+ + S_{12} V_2^+ + S_{13} V_3^+ + S_{14} V_4^+$

$V_1^- = 0 + \frac{-j}{\sqrt{2}} \cdot \frac{-j}{\sqrt{2}} \Gamma V_1^+ + \frac{-1}{\sqrt{2}} \cdot \frac{-1}{\sqrt{2}} \Gamma V_1^+ + 0$

$\boxed{V_1^- = 0} \neq \text{matched for all } \Gamma \text{ values}$

Fig.1 hand analysis analytical solution for hybrid network



## ● Simulation Circuit Schematic & Results:

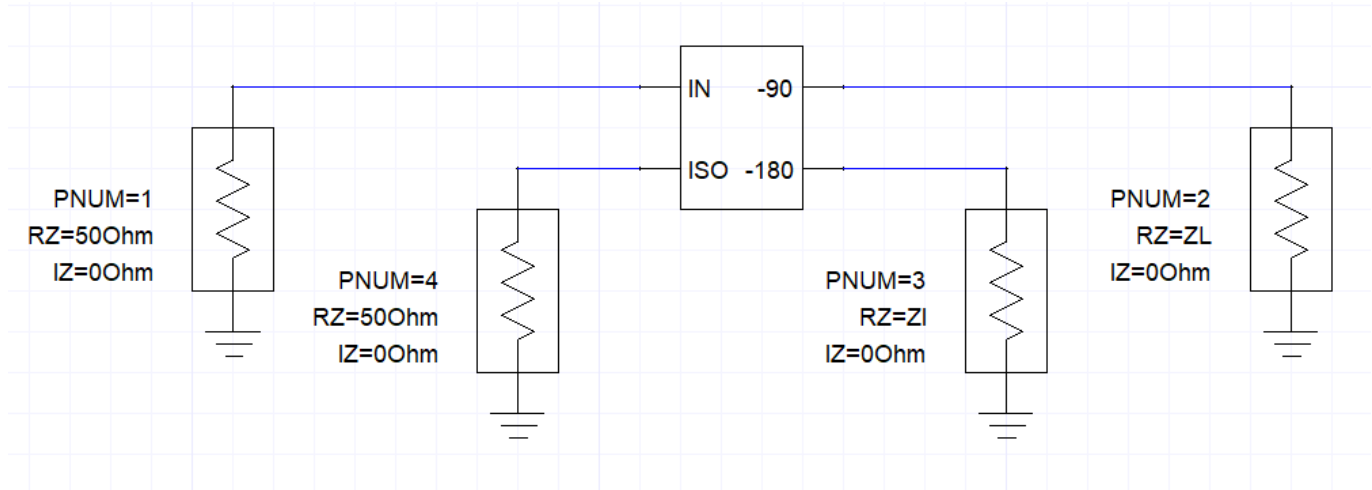


Fig.2 Circuit schematic from ANSOFT designer simulator

Now we will select the value for  $Z_l/Z_o = 5$ , so load impedance will be  $Z_l = 250 \text{ ohms}$ .

$$\text{So } T = S_{41} = J\Gamma = \frac{Z_l - Z_o}{Z_l + Z_o} = J \frac{250 - 50}{250 + 50} = J0.667 = \frac{2}{3} \angle 90^\circ.$$

30 May 2021

Ansoft Corporation  
XY Plot 1  
Circuit1

17:40:48

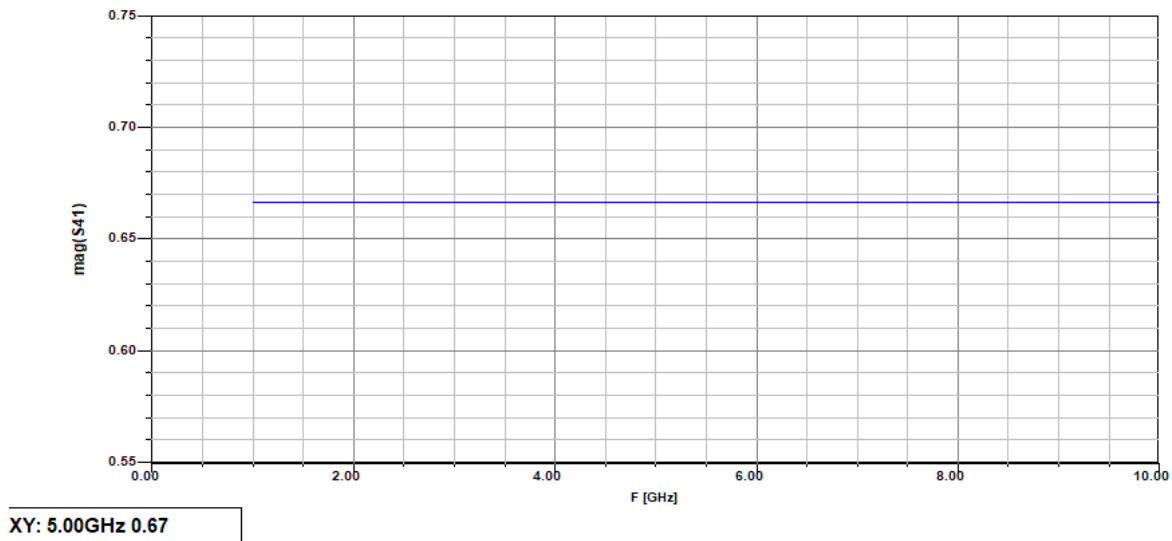


Fig.3 transmission coefficient. S41 from ANSOFT designer

Comment: so as it shown from the previous figure that  $T = J\Gamma = |S_{41}| = 0.67$ .



## • Attenuation Coefficient Vs Normalized Impedance:

Hint: I cannot draw the variation of attenuation coefficient versus normalized impedance on ANSOFT designer simulator so I do it analytically on MATLAB.

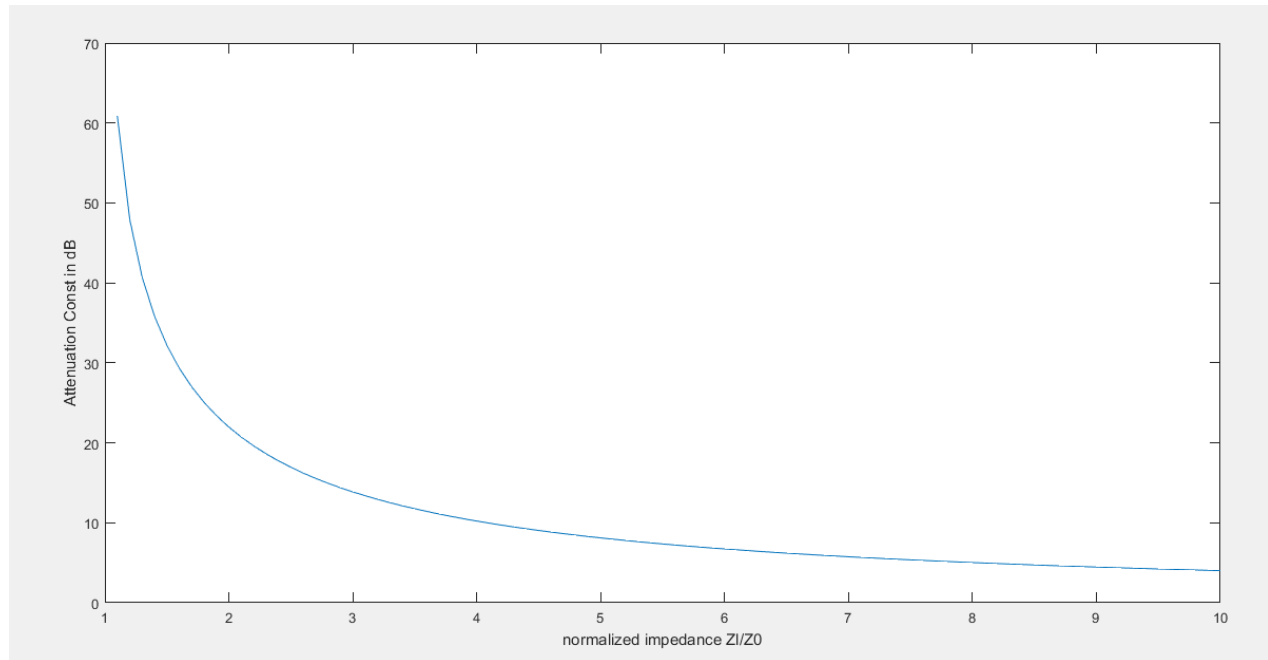


Fig.4 attenuation coefficient (S41) versus normalized impedance

## MATLAB Code:

```
clear all;
close all;

x = 1:0.1:10;          % x = Z1 / Zo
Gamma = (x-1)./(x+1);  % Gamma = S41
y = -20*log(Gamma);    % y = attenuation coeff.

figure(1);
plot(x,y)
xlabel('normalized impedance Z1/Z0');
ylabel('Attenuation Const in dB');
```